

# Electronics Laboratory

Winter semester 2025

## Lab 4 – Op Amps

Name	Jakob Haverkamp	Reg. Nr.	5932110
Name	Milan Fark	Reg. Nr.	5900383

Score and comments (only for tutors, please leave blank)

*Please fill out this cover sheet and submit it with your lab report.*

## Lab 4 - MOSFETs

11. Januar 2025

### 4.2 Non-inverting amplifier

#### 4.2.1 Simulation

##### Introduction

In this section, we simulated a non-inverting amplifier circuit shown in [Figure 5](#).

##### Circuit Diagrams:

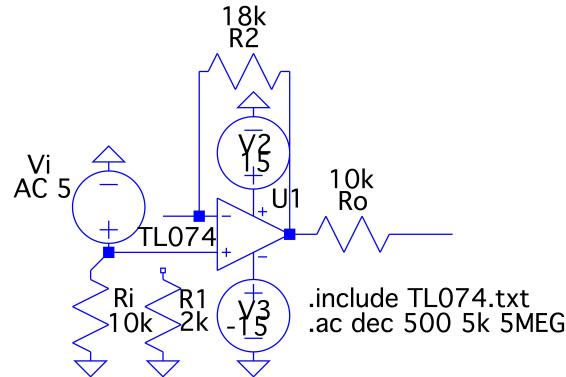


Figure 1: LTSpice *non-inverting amplifier* circuit diagram<sup>1</sup>

##### Plots:

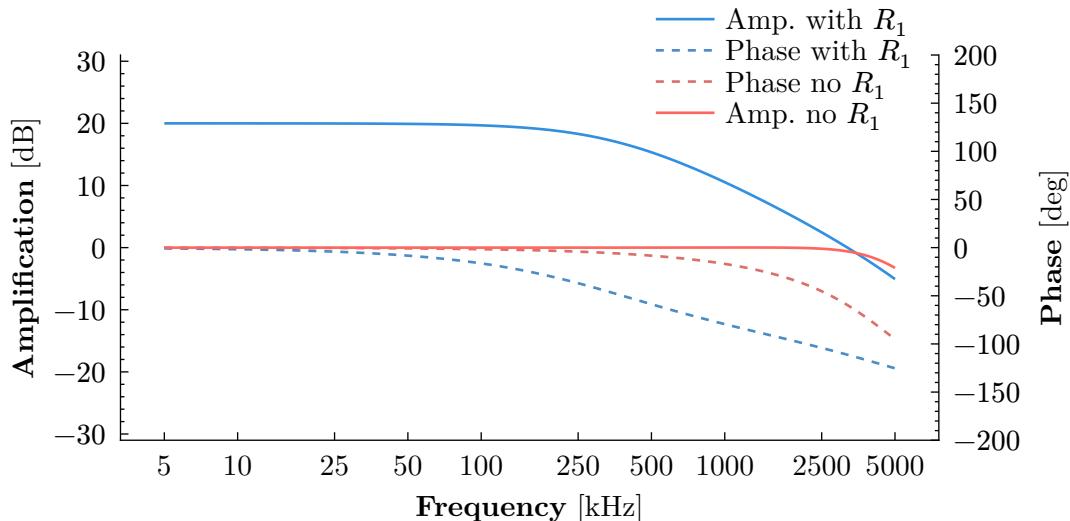


Figure 2: Simulated phase and amplification of the non-inverting amplifier for a frequency of 5kHz-5MHz on a logarithmic scale.  $R_1 = 2 \text{ k}\Omega$

<sup>1</sup>We changed AC 5 to AC 1 (so )

**Text Questions:**

**Conclusion:**

#### 4.2.2. Measurement

**Introduction**

**Circuit Diagrams:**

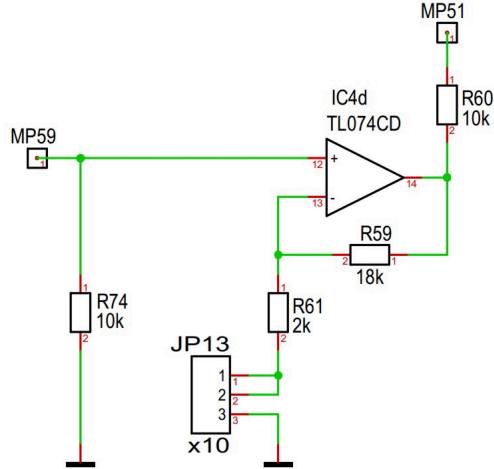


Figure 3: Schematic of the *non-inverting amplifier* circuit

**Plots:**

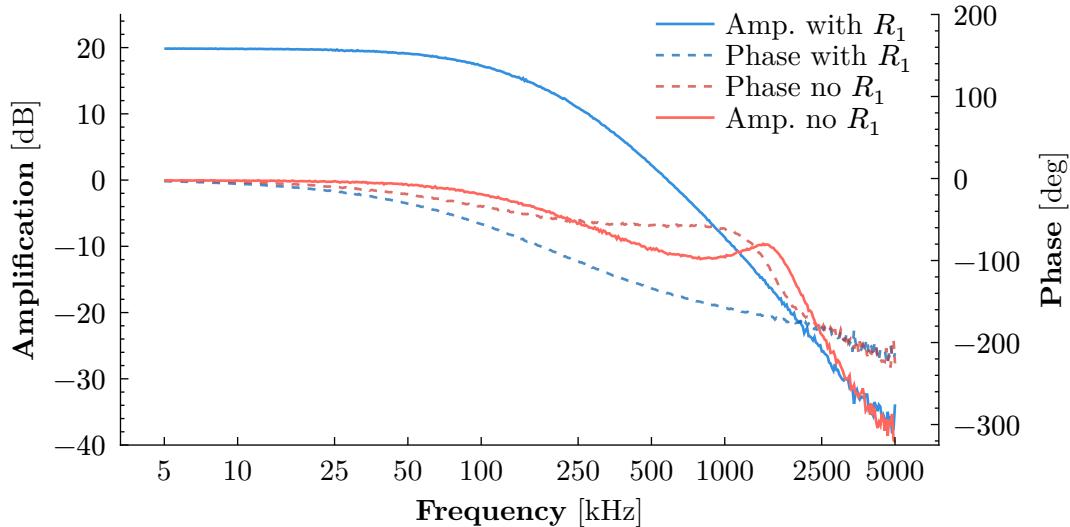


Figure 4: Simulated phase and amplification of the non-inverting amplifier for a frequency of 5kHz-5MHz on a logarithmic scale.  $R_1 = 2 \text{ k}\Omega$

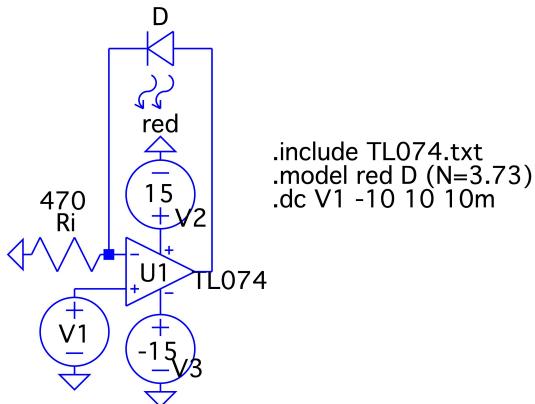
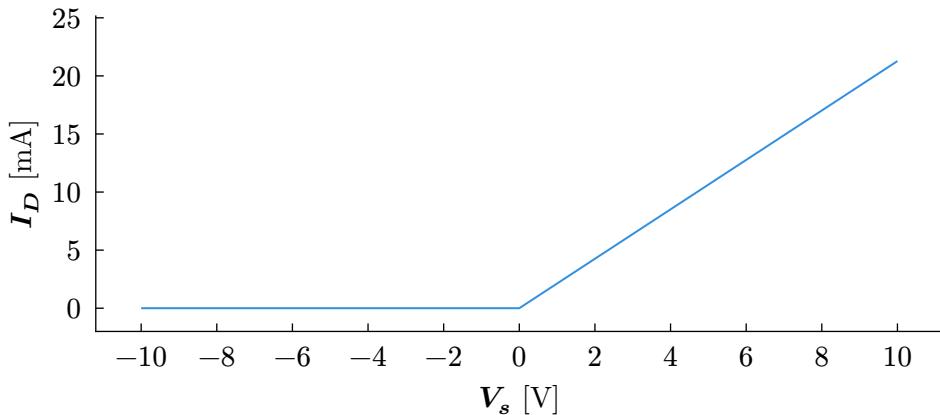
**Text Questions:****Conclusion****4.3 Voltage-to-current converter****4.3.1 Simulation****Introduction****Circuit Diagrams:**Figure 5: LTSpice *voltage-to-current converter* circuit diagram**Plots:**

Figure 6: Simulated voltage-to-current converter

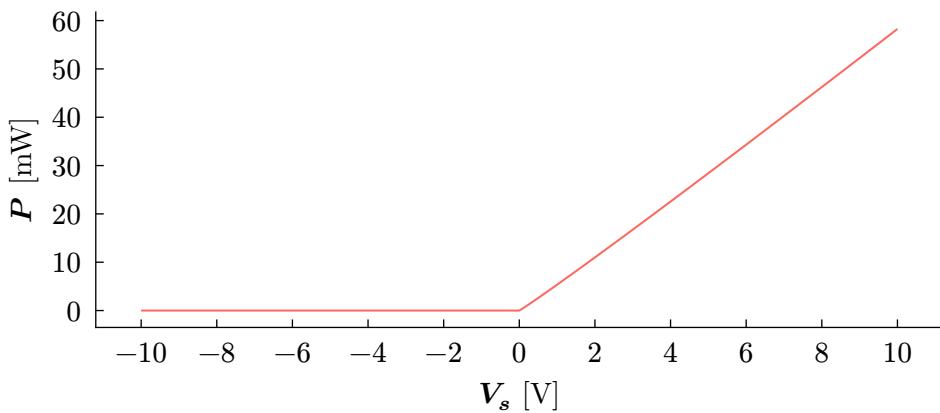
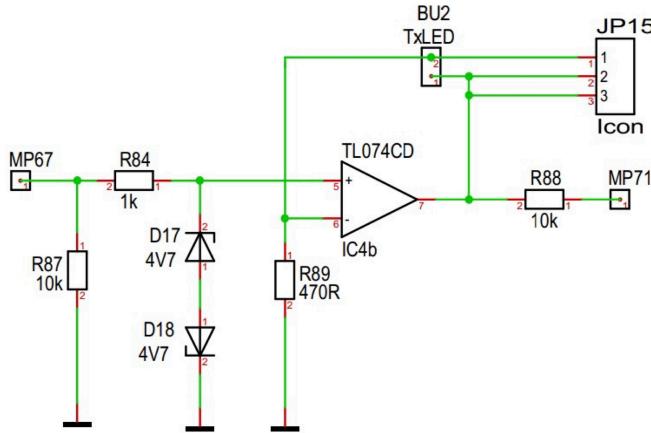
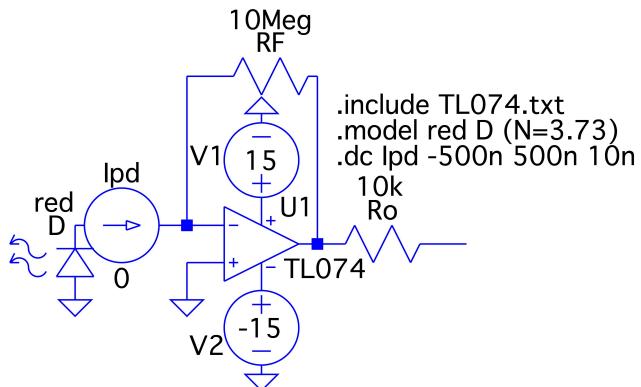


Figure 7: Simulated voltage-to-current converter

**Text Questions:****Conclusion:****4.3.2. Measurement****Introduction****Circuit Diagrams:**Figure 8: Schematic of the *voltage-to-current converter* circuit**Plots:****Text Questions:**

we took the voltage after the LED and divided by  $470 \Omega$ . Perfection.

**Conclusion****4.4 Transimpedance Amplifier****4.4.1 Simulation****Introduction****Circuit Diagrams:**Figure 9: LTSpice *transimpedance amplifier* circuit diagram

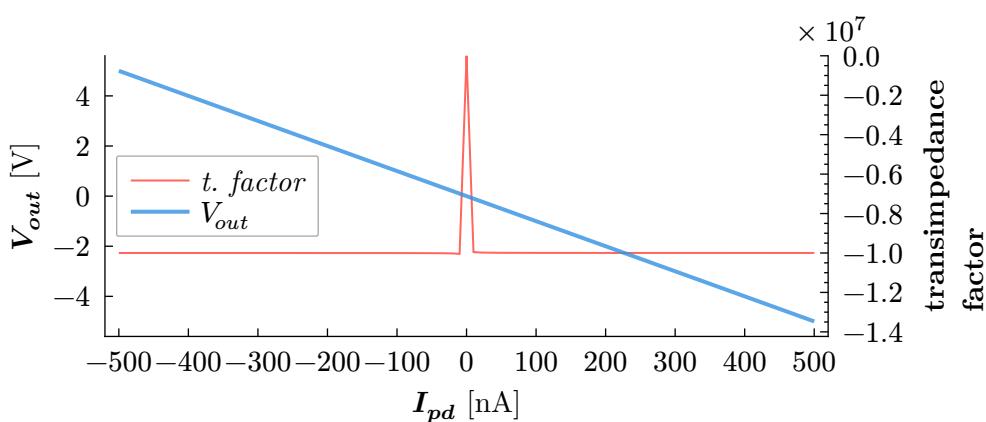
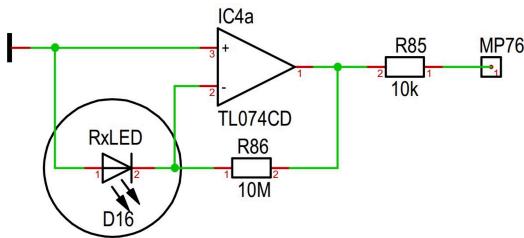
**Plots:**

Figure 10: Simulated transimpedance amplifier

**Text Questions:****Conclusion:****4.4.2. Measurement****Introduction****Circuit Diagrams:**Figure 11: Schematic of the *transimpedance amplifier* circuit**Plots:****Text Questions:**

(c) to estimate the current over D16, we use the relation  $U = -R \cdot I$  where  $R$  is  $R_{88}$  as it is inside the feedback loop of the amplifier circuit. This leads to  $I = -\frac{U}{R}$

**Conclusion**